


Programmable Electronics using FPGAs

This week


- Recap: Mealy state machine
- Moore state machine
- Vending machine controller
- Assessment 2: Traffic light controller

Recap: Mealy state machine

 - Within a Mealy machine:
 - Outputs depend on both current state and inputs
 - May be fewer states
 - It has asynchronous outputs
 - If input glitches, so does output
 - Output available immediately
 - May be unstable output




Moore state machine model

 


Moore state machine

 - In a Moore state machine:
 - Outputs depend on the current state only
 - May be more states
 - It has synchronous outputs
 - No glitch in design
 - Delay of one clock cycle
 - Stable output



Example: Vending machine controller using a Moore machine



➤ The state diagram is more complex:

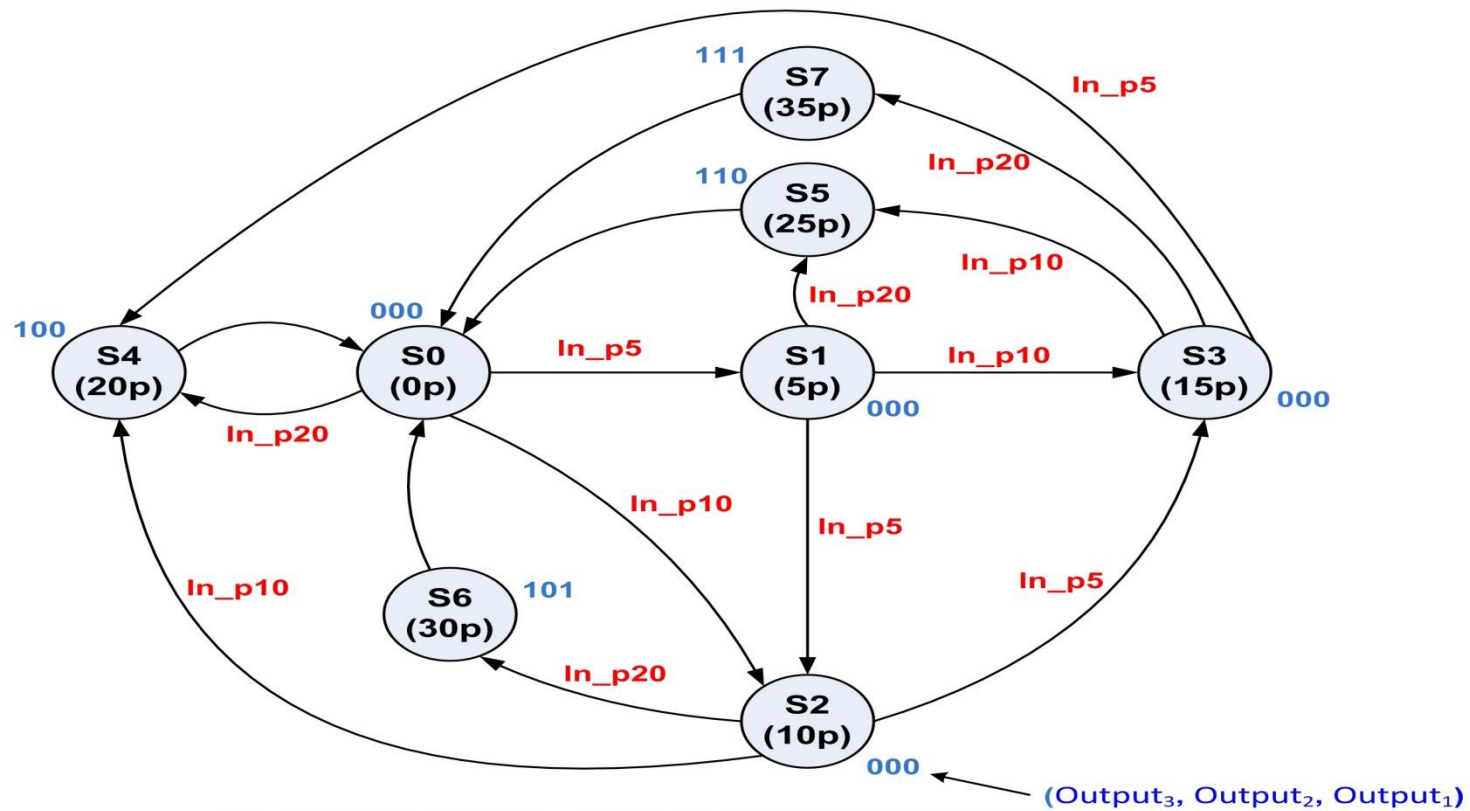

 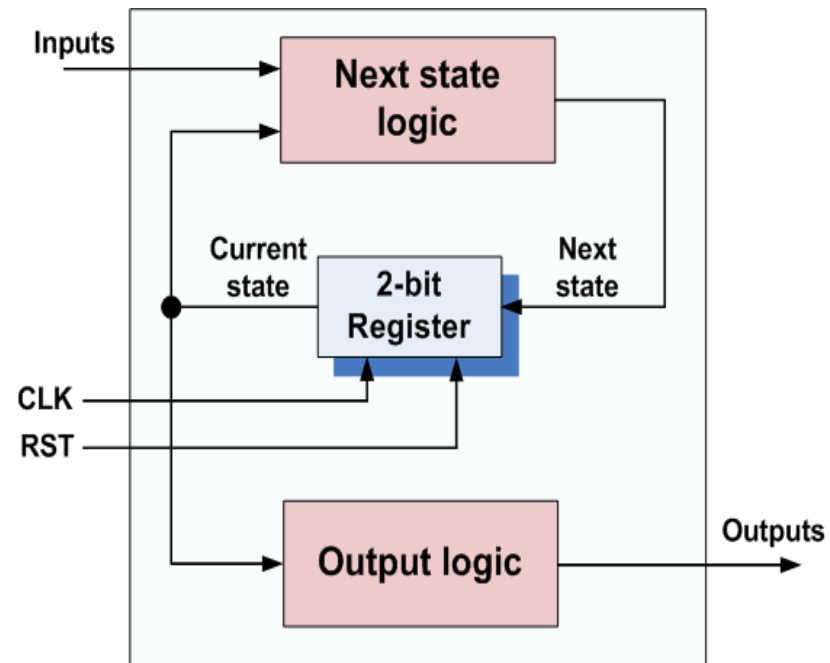Example: Vending machine controller using Moore FSM model

➤ Moore machine consists of the following components:

- Entity declaration
- Define state encoding
- State register using a process
- Next state logic using a process
- Output logic using a process



Example: Vending machine controller

- Entity declaration and define state encodings:

Entity VFSM is

```
port ( CLK, RST                : IN  std_logic;  
      In_5p, In_10p, In_20p    : IN  std_logic;  
      Dispense, Return5p, Return10p : OUT std_logic );
```

end VFSM ;

architecture My_FSM of VFSM is

```
type FSM_type is ( S0 , S1 , S2 , S3 , S4 , S5 , S6 , S7 );
```

```
signal Current_State, Next_State : FSM_type;
```

begin

Example: Vending machine controller

- State register using a process block

```
process (CLK , RST) begin
    if RST = '1' then
        Current_State <= S0;
    elsif rising_edge (CLK) then
        Current_State <= Next_State;
    else
        Current_State <= Current_State;
    end if;
end process;
```

Example: Vending machine controller

➤ Next state logic using a process block

```
process ( Current_State, In_5p, In_10p, In_20p ) begin
  case Current_State is
    when S0 => if In_5p = '1' then Next_State <= S1;
               elsif In_10p = '1' then Next_State <= S2;
               elsif In_20p = '1' then Next_State <= S4;
               else Next_State <= S0; end if;

    when S1 => ...
    when S2 => ...
    when S3 => ...
    when S4 => Next_State <= S0;
    when S5 => Next_State <= S0;
    when S6 => Next_State <= S0;
    when S7 => Next_State <= S0;
    when others => Next_State <= S0;
  end case;
end process;
```

Example: Vending machine controller

➤ Output logic using a process block

```
process ( Current_State) begin
```

```
  case Current_State is
```

```
    when S0 => Dispense <= '0'; Return5p <= '0'; Return10p <= '0';
```

```
    when S1 => Dispense <= '0'; Return5p <= '0'; Return10p <= '0';
```

```
    when S2 => Dispense <= '0'; Return5p <= '0'; Return10p <= '0';
```

```
    when S3 => Dispense <= '0'; Return5p <= '0'; Return10p <= '0';
```

```
    when S4 => Dispense <= '1'; Return5p <= '0'; Return10p <= '0';
```

```
    when S5 => Dispense <= '1'; Return5p <= '1'; Return10p <= '0';
```

```
    when S6 => Dispense <= '1'; Return5p <= '0'; Return10p <= '1';
```

```
    when S7 => Dispense <= '1'; Return5p <= '1'; Return10p <= '1';
```

```
    when others => Dispense <= '0'; Return5p <= '0'; Return10p <= '0';
```

```
  end case;
```

```
end process;
```

```
end My_FSM ;
```