


Programmable Electronics using FPGAs

This week

- Recap: A process block
- Procedural statements: wait, if-else, case, while, for
- Blocking and non-blocking statements
- How to avoid latches
- Different styles of VHDL coding
- Lab work: Identify, design, simulate and test a circuit


Recap: Process blocks

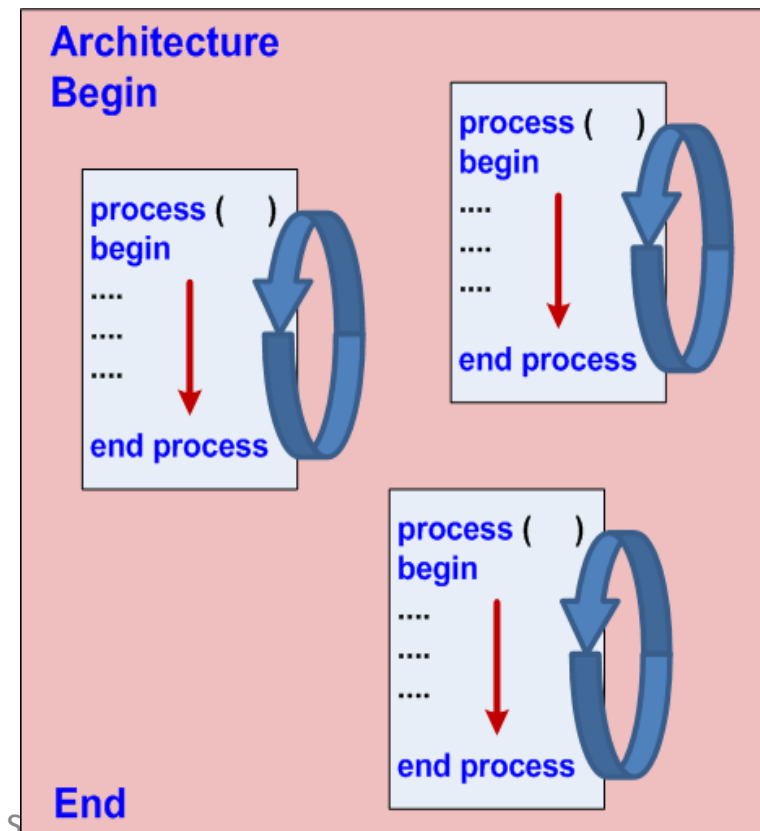- A process is the sequential composition of a number of (related) combinational logic statements.
- The statements inside a process are called procedural (sequential) statements.
- Combinatorial logic: No edge triggered logic in a process
- Sequential logic: Edge triggered logic in a process



Sequential statements: wait

 - wait statement is used:
 - To suspend the execution of a process;
 - To specify a condition when a process will be resumed;
- Not allowed in a process having sensitivity list.
- Synthesis tools ignore wait statement
- Only used in a test bench!



PROCESS BEGIN

```
A <= '0';
B <= '1';
wait for 5 ns;
```

```
A <= '1';
B <= '0';
wait until rising_edge(Clock);
```

```
A <= '0';
wait for 3 ns;
B <= '1';
```

END PROCESS;



Sequential statements: after <delay>

- after clause can be used in sequential statements to model delays in signals.
 - Expression on right-hand side will be assigned to the signal on left-hand side after the delay specified from the current time.
- Synthesis tools ignore after clauses.
- Can be observed in simulation

```

PROCESS ( Clock, Reset )
BEGIN
  IF Reset = '1' THEN
    Q <= '0';
  ELSIF rising_edge(Clock) THEN
    Q <= D after 2 ns;
  END IF;
END PROCESS;

```

  

Sequential statements: if-else

- if statement is a conditional branch.
- Based on an expression, one of two possible execution branches are chosen.

Example: 2-to-1 MUX

```
PROCESS ( A, B, S )
```

```
BEGIN
```

```
    IF S = '1' THEN
```


```
        Y <= A;
```

```
    ELSE
```

```
        Y <= B;
```

```
    END IF;
```

```
END PROCESS;
```

 

Example: DFF with reset

```
PROCESS ( Clock, Reset )
```

```
BEGIN
```

```
    IF Reset = '1' THEN
```


```
        Q <= '0';
```

```
    ELSIF rising_edge(Clock) THEN
```

```
        Q <= D;
```


```
    END IF;
```

```
END PROCESS;
```

 

Sequential statements: case

 - Based on an expression, the case statement selects one of several alternative statements for execution.
- Unlike if statement, case statement does not require a boolean expression.
- others is the default if no others are triggered.



Example: 4-to-1 MUX

```

PROCESS ( A, B, C, D, Sel )
BEGIN
    CASE Sel IS
        when "000" => Y <= A;
        when "001" => Y <= B;
        when "010" => Y <= C;
        when "011" => Y <= D;
        when others => Y <= '0';
    END CASE;
END PROCESS;

```

Sequential statements: *while loop*


- A while loop statement is a conditional loop statement. It executes until the condition becomes false.
- Beware of using while loops in RTL design, as there may be a hidden impact on clock speed.

Example: A while loop in a process

```

PROCESS
BEGIN
    while i <= 3 loop
        wait until rising_edge(Clock);
        i <= i + 1;
    end loop;
END PROCESS;

```

 


Sequential statements: for loop

- A for loop statement executes one or more statements repeatedly a fixed number of times.

 Example: A for loop in a process


```
PROCESS
BEGIN
    for i in 0 to 3 loop
        wait until rising_edge(Clock);
    end loop;
END PROCESS;
```



Non-blocking sequential statements

- Signal assignment statements are executed sequentially, but are also non-blocking!
 - *signal* \leftarrow *expression*;
 - Signals have no intermediate values.
- We could have written RTL as two concurrent processes.

 Question – how can you swap the value of two variables?



Architecture RTL of ShfReg is

```

signal dff1, dff2 : STD_LOGIC;
begin
  process(Clock, Reset)
  begin
    if Reset = '1' then
      dff1 <= '0';
      dff2 <= '0';
    elsif rising_edge(Clock) then
      dff1 <= Din;
      dff2 <= dff1;
    end if;
    Dout <= dff2;
  end process;
End RTL;
  
```

Blocking sequential statements

- The keyword variable can be used to store intermediary results in a process.
 - Declared and used within a process block only – not globally in an architecture
- Variable assignment statements are blocking
 - *variable* **:=** *expression*;

```
PROCESS (A)
variable X, Y, Z : std_logic := "00";
BEGIN
    X := A ;
    Y := X + 1;
    Z := X + Y ;
END PROCESS;
```



**Assume A is 1 before entering
in this process block**

**At the end of process block,
X will be 1
Y will be 2
Z will be 3**

Blocking sequential statements

Architecture RTL of ShfReg is

begin

process(Clock, Reset)

variable dff1, dff2 : STD_LOGIC;

begin

if Reset = '1' then

dff1 := '0';

dff2 := '0';

elsif rising_edge(Clock) then

dff1 := Din;



dff2 := dff1;

end if;

Dout <= dff2;

end process;

End RTL;

  

How to avoid latches?

- All input signals of a process must be mentioned in its sensitivity list.
- if statement must be completely specified – there must be an else clause present.
- Incomplete if statements or sensitivity lists may create a latch.
- Unlike DFF a latch is a level-trigger storage.
- We should avoid latches in FPGA designs, as they may lead to timing problems.



Example: **PROCESS (A)** -- *Here B is missing in sensitivity list.*
BEGIN
 Y <= A AND B;
END PROCESS;

How to avoid latches?

```

PROCESS ( A, B, S )
BEGIN
    if S = '1' then
        Y <= A AND B;
    end if;
END PROCESS;



```

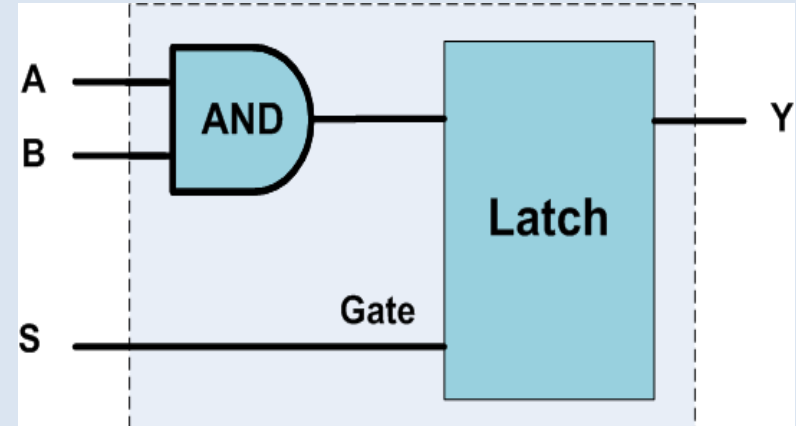 

```


PROCESS ( A, B, S )
BEGIN
    if S = '1' then
        Y <= A AND B;
    else
        Y <= A OR B;
    end if;
END PROCESS;

```

  

Different styles of VHDL coding

 - A circuit can be designed using different styles in VHDL without compromising the resources.



Example: Half-adder using dataflow modelling

Architecture RTL of HalfAdd IS
BEGIN

Sum <= in1 **XOR** in2;

Cout <= in1 **AND** in2;

END RTL;

Example: Half-adder using behavioural modelling

Architecture RTL of HalfAdd IS
BEGIN

PROCESS (in1, in2)
BEGIN


Sum <= in1 **XOR** in2;

Cout <= in1 **AND** in2;


END PROCESS;

END RTL;

Different styles of VHDL coding

 

OR

 

Example: MUX using dataflow modelling

Architecture RTL of Mux IS
BEGIN

```
n1 <= NOT S;
a1 <= A AND n1;
a2 <= B AND S;
Y <= a1 OR a2;
```

END RTL;

Example: MUX using behavioural modelling

Architecture RTL of Mux IS
BEGIN

```
PROCESS ( A, B, S )
BEGIN
```

```
    if S = '0' then
```

```
        Y <= A;
```

```
    else
```

```
        Y <= B;
```

```
    end if;
```

```
END PROCESS;
```

END RTL;

Lab work: Identify, design, simulate, and test a circuit

- **Step 1:** Represent this circuit using Boolean expressions and a truth table.
- **Step 2:** Implement this circuit in VHDL firstly using dataflow modelling, and secondly using behavioural modelling.
- **Step 3:** Create a test bench and compare the simulation with your truth table.
- **Step 4:** Implement your design on the FPGA board.

