

Programmable Electronics using FPGAs

This week

- VHDL essentials - data objects and their types
- Hierarchical design
- Abstraction levels – Structural modelling
- Component instantiation
- Connecting ports
- Lab work 1: Design a 1-bit Full Adder
- Lab work 2: Design a 2-bit Full Adder

Data objects

- Three types of data objects are used in VHDL:
 - Signals
 - Constants
 - Variables
- Signals are most commonly used to describe the logic circuit. They represent the wires of the circuit.
- Constants are used to define a value which cannot be changed.
- Variables are usually used to store computational data within a procedural block. They do not necessarily represent a wire in a circuit.

Data object values and numbers

- bit values: '0', '1'
- boolean values: TRUE, FALSE
- integer values: 152, 1, 9 etc
- std_logic values: U, X, -, Z, H, L, 0, 1:
 - **U** = uninitialized
 - **X** = - = don't care
 - **Z** = undefined voltage range
 - **H/L** = weak 0 or 1 – can't be trusted in VHDL!
- std_logic_vector values: b"00101101" , b"1101" , x"A07B" etc

STD_LOGIC and STD_LOGIC_VECTOR

- STD_LOGIC is used for single bit signals
- STD_LOGIC_VECTOR is used for multi-bit signals (words).

For example :

```
signal X std_logic;  
signal Y std_logic_vector(3 downto 0);  
signal Z std_logic_vector(0 upto 5);
```


- STD_LOGIC_VECTOR is also bit accessible.
 - Individual bits can be accessed, just like an array.
- The least significant bit is the one indexed **0** in the declaration.

For example : $Y \leq "0101";$


Here $Y(0) = 1$, $Y(1) = 0$, $Y(2) = 1$ and $Y(3) = 0$

Hierarchical design

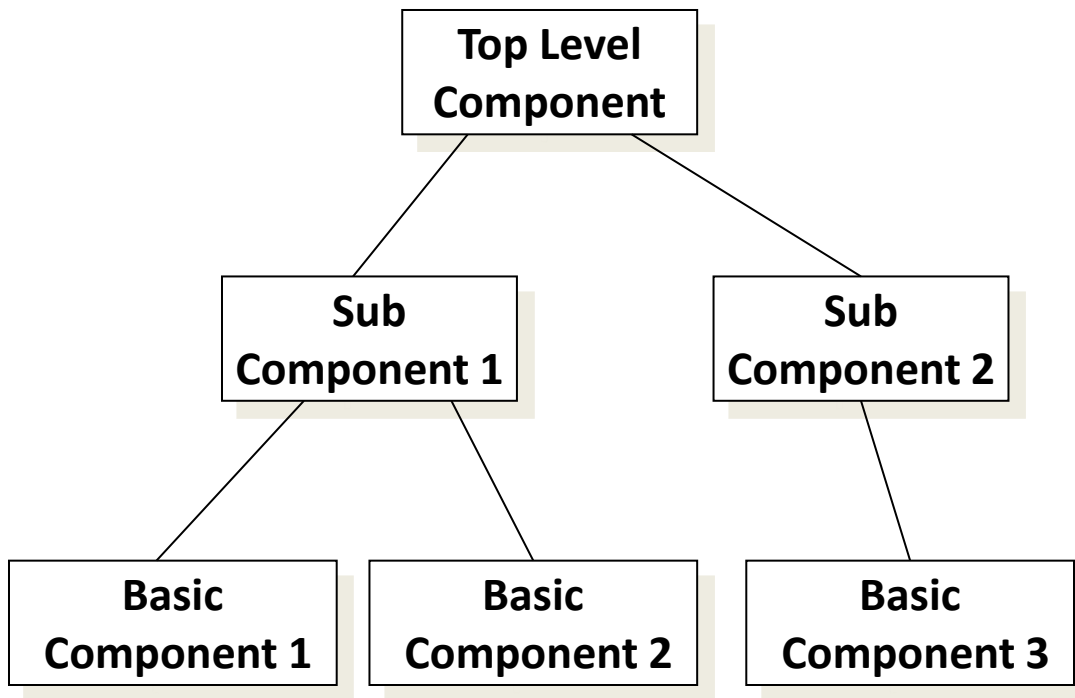- We often build a digital system using existing components.



 For example : A full adder consists of two half adders



Abstraction levels: Structural Modelling

- Structural modelling is used to connect (instantiate) existing components with each other.
- It describes the arrangement and interconnections of components via their ports.
- Structural modelling is performed in two steps:
 1. Component instantiation
 2. Connecting ports

Step 1: Component instantiation

- Entity/architecture pairs can be declared as a “component”
- This allows us to treat them as black boxes in larger designs.

For example : AND gate


```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY MyAND IS
PORT (
    X,Y : IN STD_LOGIC;
    Z : OUT STD_LOGIC
);
END MyAND;

ARCHITECTURE dataflow of MyAND IS
Begin
    Z <= X AND Y;
end dataflow;

```

 

```

COMPONENT MyAND IS
    PORT (
        X : IN STD_LOGIC;
        Y : IN STD_LOGIC;
        Z : OUT STD_LOGIC
    );
END COMPONENT;

```


Step 1: Component instantiation

- VHDL models consist of hierarchy of component instances.


For example:

MyAND3 consists of 3 MyAND instances U1, U2, and U3 with the pins connected together:

```
U1: MyAND port map (Port connections...);
```


```
U2: MyAND port map (Port connections...);
```
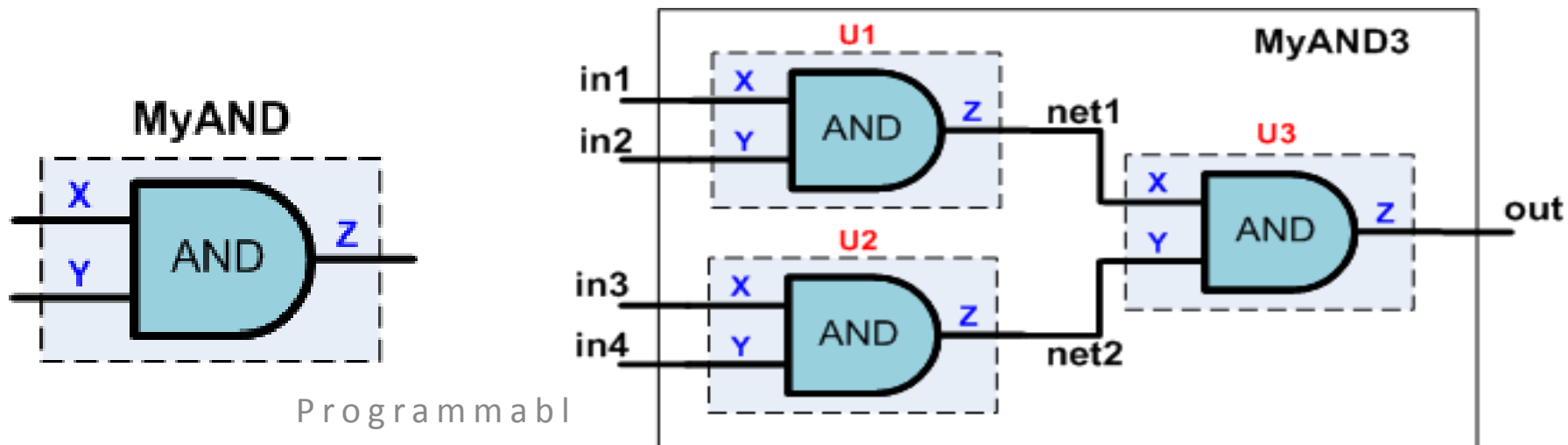
```
U3: MyAND port map (Port connections...);
```



Step 2: Connecting ports

 - Components can be connected together by specifying the component names of each specific pin



For example :

MyAND3 consists of 3 MyAND

gates U1, U2, and U3 with the pins connected together:

```

U1: MyAND port map (X => in1, Y => in2, Z => net1);
U2: MyAND port map (X => in3, Y => in4, Z => net2);
U3: MyAND port map (X => net1, Y => net2, Z => out);
  
```

Example: Hierarchical circuit design

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY MyAND3 IS
    PORT (
        in1,in2,in3,in4 : IN STD_LOGIC;
        out : OUT STD_LOGIC);
END MyAND3;

```

```

ARCHITECTURE structural of MyAND3 IS
    COMPONENT MyAND IS
        PORT (
            X : IN STD_LOGIC;
            Y : IN STD_LOGIC;
            Z : OUT STD_LOGIC);
    END COMPONENT;

```

```

    signal net1, net2 : STD_LOGIC;
    Begin

```

```


        U1: MyAND port map (X => in1, Y => in2, Z => net1);
        U2: MyAND port map (X => in3, Y => in4, Z => net2);
        U3: MyAND port map (X => net1, Y => net2, Z => out);

```

```

    end structural;



```

 

Lab work 1: Designing a 1-bit full adder

- A full adder consists of two half adders and an OR gate.
- These circuits operate side by side.

Example: 1-bit full adder

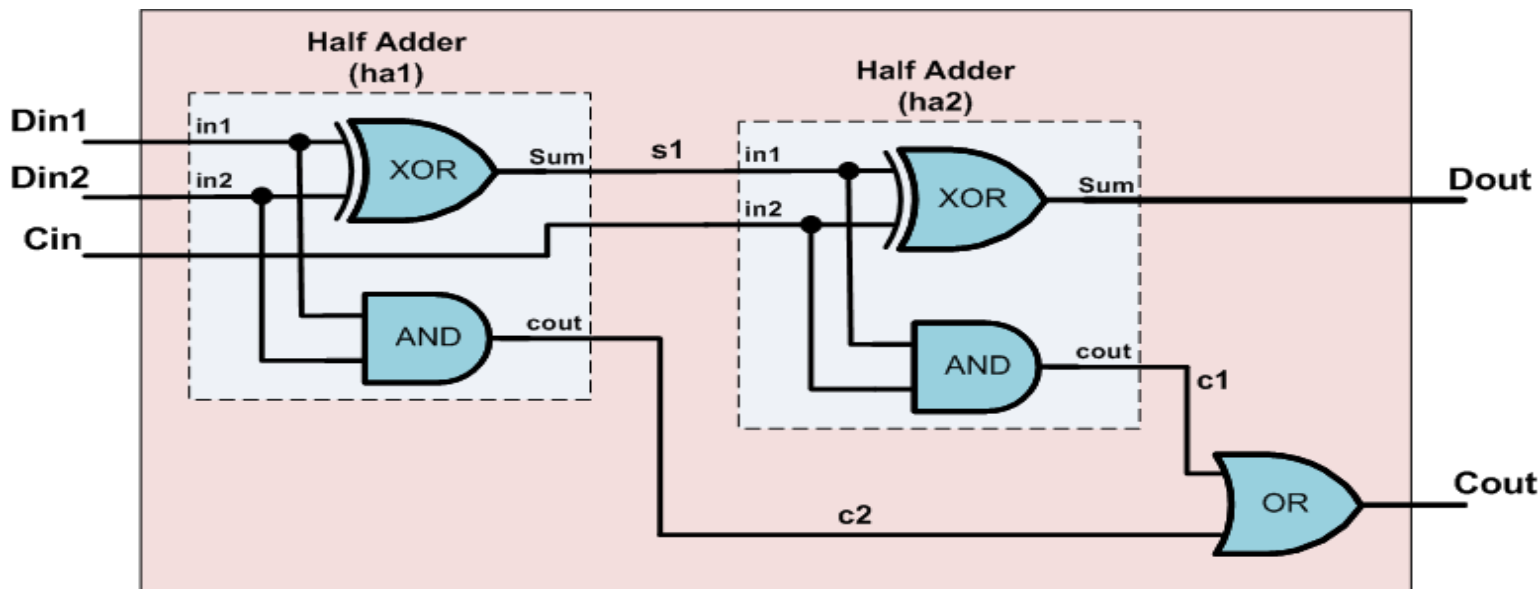 


Lab work 1: Designing a 1-bit full adder

- Use your half adder design as a component.
- You need one concurrent statement and two instantiations in an architecture.
 - Concurrent statement is for OR gate.
 - One instantiation per a half adder component.

Hints: Use dataflow level for OR gate and structural level for instantiation of two half adders

```
-- For OR gate
Cout <= c1 OR c2;
```
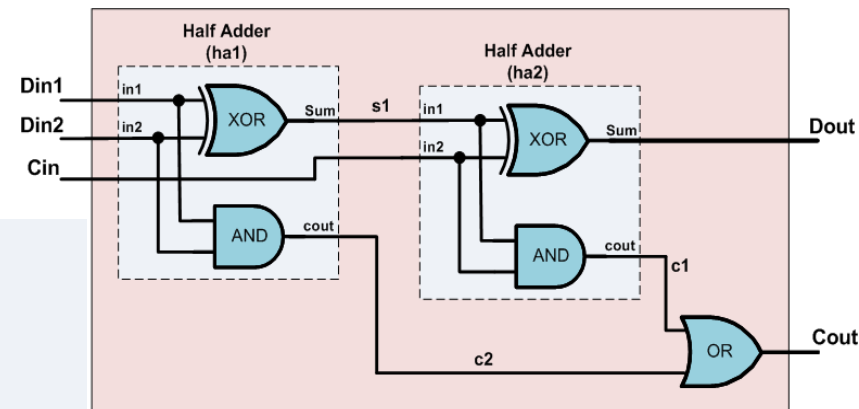
```
-- Instantiation of a half adder
ha1: HalfAdder port map(
    in1 => Din1,
    in2 => Din2,
    Sum => s1,
    cout => c2
);
```



Lab work 2: Designing a 2-bit full adder

- A 2-bit full adder can be designed using two 1-bit full adders.
- Follow the same rule as for 1-bit full adder design.

Example:
2-bit full adder

